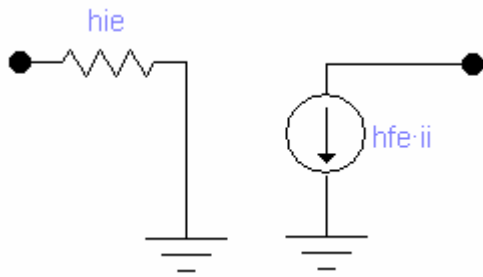


# FORMULARIO ELETTRONICA

## QUADRIPOLI

### TRANSISTOR A EMETTITORE COMUNE



$$R_i = h_{ie}$$

$$R_u = \infty$$

$$A_v = -\frac{R_{pc}}{R_i} A_i$$

$$A_{v_{tot}} = \frac{V_u}{V_s} = A_v \cdot \alpha_v$$

$$\alpha_v = \frac{R_{it}}{R_{it} + R_s}$$

$$A_i = h_{fe}$$


$$R_{pc} = \text{Resistenza destra}$$

$$V_u = V_s \cdot A_{v_{tot}}$$

$$V_{e_q} = V_{AB} + R_{ut} I_1$$

$$V_{ce_{tot}} = V_{ce_q} + V_{u(t)}$$

### TRANSISTOR A COLLETTORE COMUNE

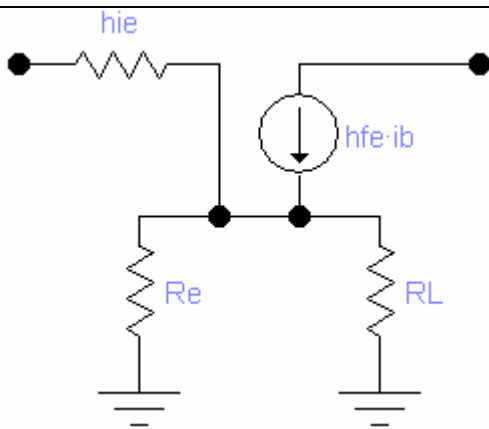

$$R_i = h_{ie} + A_i \cdot R_{pe}$$

$$R_u = \frac{h_{ie} + R_s}{h_{fe} + 1}$$

$$A_v = \frac{R_{pe} \cdot A_i}{R_i}$$

$$A_{v_{tot}} = \frac{V_u}{V_s} = A_v \cdot \alpha_v$$

$$\alpha_v = \frac{R_{it}}{R_{it} + R_s}$$

$$R'_s = h_{ie} + R_s // (R_1 // R_2)$$

$$R_{it} = R_i // R_b$$


$$R_{ut} = R_u // R_e$$

$$R_{pe} = \text{Resistenza sotto } (R_e // R_l)$$

$$A_i = h_{fe} + 1$$

$$A_{i_{tot}} = \frac{V_u / R_L}{V_i / R_{it}}$$

### TRANSISTOR A BASE COMUNE

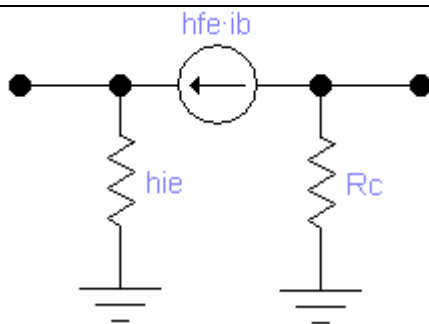

$$R_i = \frac{h_{ie}}{h_{fe} + 1}$$

$$R_u = \infty$$

$$A_v = -\frac{R_{pc}}{R_i} \cdot A_i \cong \frac{R_{pc}}{R_i}$$

$$A_i = \frac{I_u}{I_i} = \frac{I_c}{I_e} \cong -1$$

$$R_{pc} = \text{Resistenza a dx del generatore } h_{fe} \cdot i_b$$

$$R_{it} = R_e // h_{ie}$$

$$A_{v_{tot}} = A_v \cdot \alpha_v$$

$$\alpha_v = \frac{R_{it}}{R_{it} + R_s}$$

### TRANSISTOR A DOPPIO CARICO

$$R_i = h_{ie} + h_{fe} \cdot R_{pe}$$

$$R_{pc} = R_c // R_L$$

$$A_{vc} = -\frac{R_{pc} \cdot A_{ic}}{R_i}$$

$$R_{uc} = \infty$$

$$A_{ic} \cong h_{fe}$$

$$A_{ie} \cong h_{fe}$$

$$A_{ve} = \frac{R_{pe} \cdot A_{ie}}{R_i}$$

$$R_{ue} = \frac{h_{ie} + R'_s}{h_{fe}}$$


$$R_{pe} = R_e // R_l$$

$$R_{pl} = R_c // R_l$$

$$R'_s = \text{resistenza a sinistra del transistor}$$

## JFET A SOURCE COMUNE

( $g_m$  è un parametro dato)

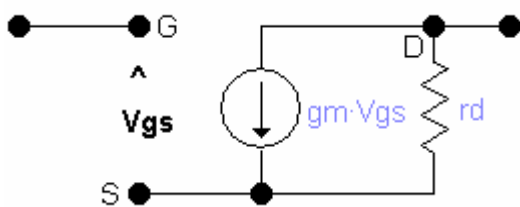

$$R_i = \infty$$

$$R_u = r_d$$

$$A_v = -g_m \cdot r_d // R_{pd}$$

$$\alpha_v = \frac{R_{it}}{R_{it} + R_s}$$

$$A_i = \infty$$


$$R_{it} = R_g$$

$$R_{ut} = r_d // R_{pd}$$

$$A_{v_{tot}} = A_v \cdot \alpha_v$$

$$A_{it} = A_v \cdot \frac{R_g}{R_l}$$

## JFET A DRAIN COMUNE

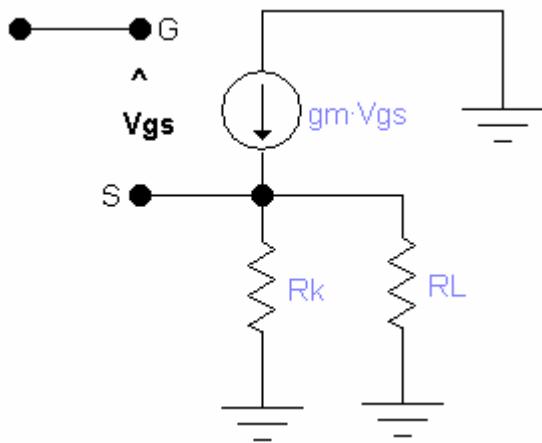

$$R_i = \infty$$

$$R_u = \frac{1}{g_m}$$

$$A_v = \frac{R_k // R_l \cdot g_m}{1 + g_m \cdot R_k // R_l}$$


$$A_i = \infty$$

$$R_{it} = R_g$$

$$R_{ut} = R_u // R_k$$

$$A_{v_{tot}} = A_v \cdot \alpha_v$$

## JFET A GATE COMUNE

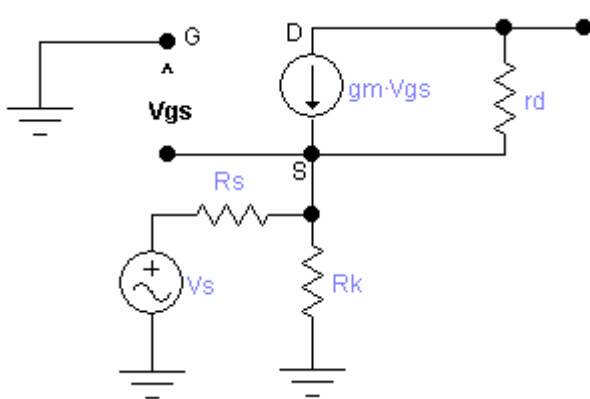

$$R_i = \frac{1}{g_m}$$

$$R_u = r_d (1 + R'_s (1 + g_m \cdot r_d))$$

$$A_i = -1$$

$$A_v = \frac{R_{pd}}{R_i} \cong g_m \cdot R_{pd}$$

$$A_{v_{tot}} = A_v \cdot \alpha_v$$

$$R_{ut} = R_u // R_d$$

$$V_{gs} = V_p \left( 1 - \sqrt{\frac{I_{ds}}{I_{dss}}} \right)$$

$$I_{ds} = I_{dss} \left( 1 - \frac{V_{gs}}{V_p} \right)^2$$

$$h_{fe} = \frac{I_c}{I_b}$$

NB

NON MI RITENGO RESPONSABILE SE LA VERIFICA VA MALE



Sito web: [www.lucam91.altervista.org](http://www.lucam91.altervista.org)

E-Mail: [lucam91@gmail.com](mailto:lucam91@gmail.com)